

## CH # 16 ELECTRICITY

Some important formulae:

$$\begin{aligned} \text{i) } \Delta V &= \frac{W_{AB}}{q} & \text{ii) } \frac{1}{R} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ \text{iii) } V &= IR & \text{iv) } R &= R_1 + R_2 + R_3 & \text{v) } P &= IV \end{aligned}$$

**16.1:** Calculate the amount of work done in carrying a charge of  $+2.5\mu\text{C}$  from A to B, if A is a potential of  $-60\text{V}$  and B is at  $+10\text{V}$ .

*GIVEN:*

$$\text{Charge} = q = +2.5\mu\text{C} = +2.5 \times 10^{-6}\text{C}$$

$$\text{Electric potential at point A} = V_A = -60\text{V}$$

$$\text{Electric potential at point B} = V_B = +10\text{V}$$

*REQUIRED:*

$$\text{Work done of charge from A to B} = W_{AB} = ?$$

*SOLUTION:*

$$\Delta V = \frac{W_{AB}}{q}$$

$$W_{AB} = \Delta V \times q$$

$$W_{AB} = (V_B - V_A) \times q$$

$$W_{AB} = \{10 - (-60)\} \times 2.5 \times 10^{-6}$$

$$W_{AB} = 70 \times 2.5 \times 10^{-6}$$

$$W_{AB} = 1.75 \times 10^{-4}\text{J}$$

**16.2:** Find the potential difference between the two ends of the conductor if it offers a resistance of  $5\Omega$ . Take the current flowing through the conductor as 5 amperes.

*GIVEN:*

$$\text{Resistance} = R = 5\Omega$$

$$\text{Current} = I = 5\text{A}$$

*REQUIRED:*

$$\text{Potential difference} = V = ?$$

*SOLUTION:*

According to Ohm's law,

$$V = IR$$

$$V = (5)(5)$$

$$V = 25\text{V}$$

**16.3:** The potential difference applied to the terminals of a portable radio is 9Volts. Find the resistance of the radio if a current of 25mA is flowing through it.

*GIVEN:*

$$\text{Potential difference} = V = 9\text{V}$$

$$\text{Current} = I = 25\text{mA} = 25/1000 = 0.025\text{A}$$

*REQUIRED:*

$$\text{Resistance} = ?$$

*SOLUTION:*

According to Ohm's law,

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{9}{0.025}$$

$$R = 360\Omega$$

**16.4:** An electric toaster has a resistance of  $12\Omega$ . What current will it drawn from a 120V supply?

*GIVEN:*

$$\text{Resistance} = R = 12\Omega$$

$$\text{Potential difference} = V = 120\text{V}$$

*REQUIRED:*

$$\text{Electric current} = I = ?$$

*SOLUTION:*

According to Ohm's law,

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{120}{12}$$

$$I = 10\text{A}$$

**16.5:** A series circuit consists of three resistances of  $40\Omega$ ,  $50\Omega$  and  $20\Omega$  respectively is connected across a voltage source of 120V as shown in figure. Find the

current in the circuit and potential difference across each resistor.

GIVEN:

$$\text{Resistance} = R_1 = 40\Omega$$

$$\text{Resistance} = R_2 = 50\Omega$$

$$\text{Resistance} = R_3 = 20\Omega$$

$$\text{Voltage} = V = 120V$$

REQUIRED:

$$\text{Current in circuit} = I = ?$$

$$\text{Potential difference across each resistor} = V_1, V_2, V_3 = ?$$

SOLUTION:

Equivalent resistance:

$$R = R_1 + R_2 + R_3$$

$$R = 40 + 50 + 20$$

$$R = 110\Omega$$

Current in circuit:

According to Ohm's law,

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{120}{110}$$

$$I = 1.09A$$

Potential difference across  $R_1$ :

$$V_1 = IR_1$$

$$V_1 = (1.09)(40)$$

$$V_1 = 43.64V$$

Potential difference across  $R_2$ :

$$V_2 = IR_2$$

$$V_2 = (1.09)(50)$$

$$V_2 = 54.55V$$

Potential difference across  $R_3$ :

$$V_3 = IR_3$$

$$V_3 = (1.09)(200)$$

$$V_3 = 21.82V$$

16.6: Resistors of  $4\Omega$ ,  $6\Omega$  and  $12\Omega$  are connected in parallel and then joined to an EMF source of  $6V$ . Find the value of:

i) The equivalent resistance of the circuit.

ii) The total current flowing in the circuit.

iii) The current passing through each resistance.

GIVEN:

$$\text{Resistance} = R_1 = 4\Omega$$

$$\text{Resistance} = R_2 = 6\Omega$$

$$\text{Resistance} = R_3 = 12\Omega$$

$$\text{Voltage} = V = 6V$$

REQUIRED:

i) Equivalent resistance =  $R = ?$

ii) Current in circuit =  $I = ?$

iii) Current flowing through each resistor =  $I_1, I_2, I_3 = ?$

SOLUTION:

Equivalent resistance:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12}$$

$$\frac{1}{R} = \frac{3 + 2 + 1}{12}$$

$$\frac{1}{R} = \frac{6}{12}$$

$$\frac{1}{R} = \frac{1}{2}$$

$$R = 2\Omega$$

Current in circuit:

According to Ohm's law,

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{6}{2}$$

$$I = 3A$$

Current flow through  $R_1$ :

$$V = I_1 R_1$$

FAHAD AKHTER

$$I_1 = \frac{V}{R_1}$$

$$I_1 = \frac{6}{4}$$

$$I_1 = 1.5A$$

Current flow through R<sub>2</sub>:

$$V = I_2 R_2$$

$$I_2 = \frac{V}{R_2}$$

$$I_2 = \frac{6}{6}$$

$$I_2 = 1A$$

Current flow through R<sub>3</sub>:

$$V = I_3 R_3$$

$$I_3 = \frac{V}{R_3}$$

$$I_3 = \frac{6}{12}$$

$$I_3 = 0.5A$$

**16.7: Two light bulbs of 100watt and 60watt both operate in a 220V circuit. Which bulb has the higher resistance and which bulb carries greater current.**

*GIVEN:*

$$\text{Power} = P_1 = 100W$$

$$\text{Power} = P_2 = 60W$$

$$\text{Voltage} = 220V$$

*REQUIRED:*

$$\text{Higher resistance} = R = ?$$

$$\text{Greater current} = I = ?$$

*SOLUTION:*

For 100Watt bulb:

Current,

$$P = IV$$

$$I = \frac{P}{V}$$

$$I = \frac{100}{220}$$

$$I = 0.4545A$$

Resistance,

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{220}{0.4545}$$

$$R = 488.88\Omega$$

For 60Watt bulb:

Current,

$$P = IV$$

$$I = \frac{P}{V}$$

$$I = \frac{60}{220}$$

$$I = 0.2727A$$

Resistance,

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{220}{0.2727}$$

$$R = 806.66\Omega$$

By comparing both bulbs,

Higher resistance = 60Watt bulb

Greater current = 100Watt bulb

**FAHAD AKHTER**